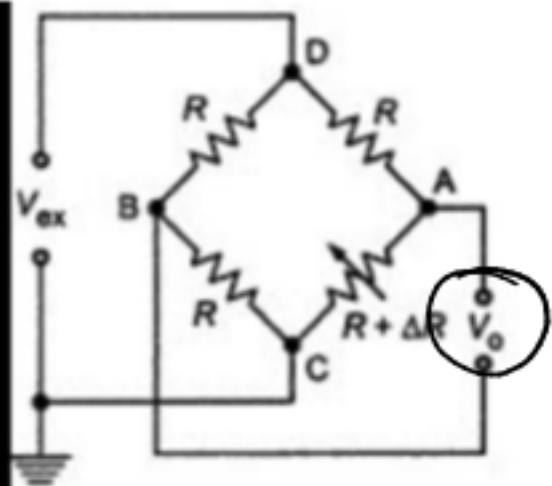



Lecture 5

Potentiometric circuits.


Wheatstone bridge




Quarter-bridge

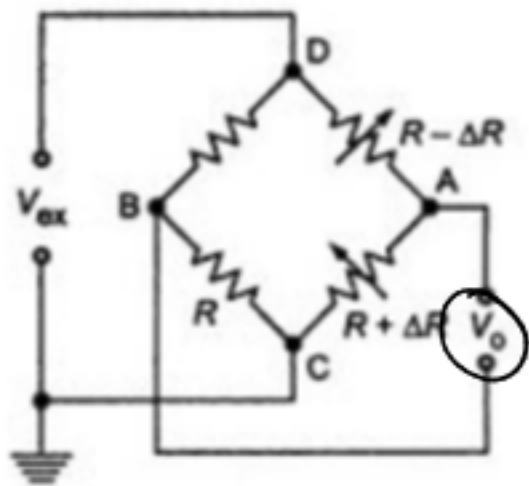

Half-bridge

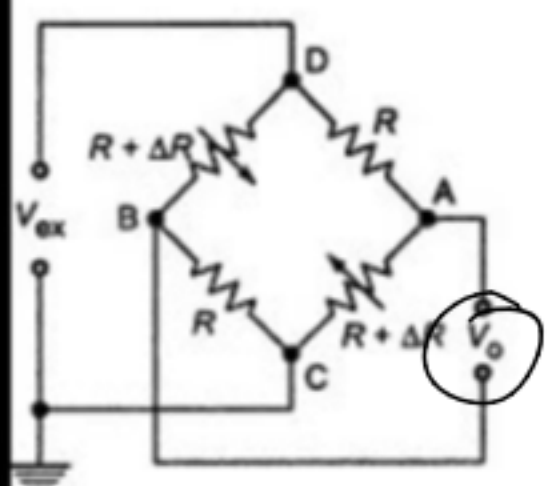


Half-bridge

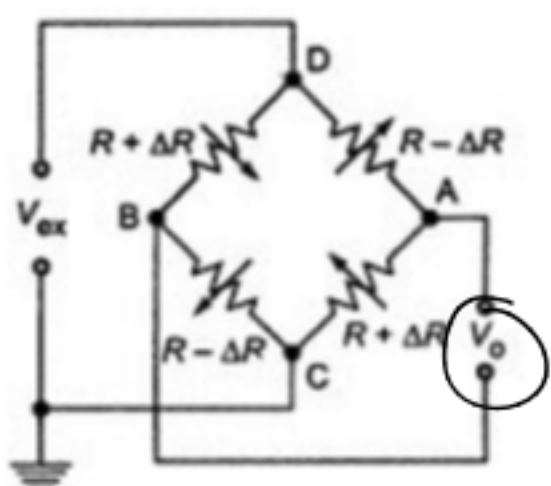

Full-bridge

Q. Given a balanced bridge, how do changes in the resistances of the various

elements affect the voltmeter reading.

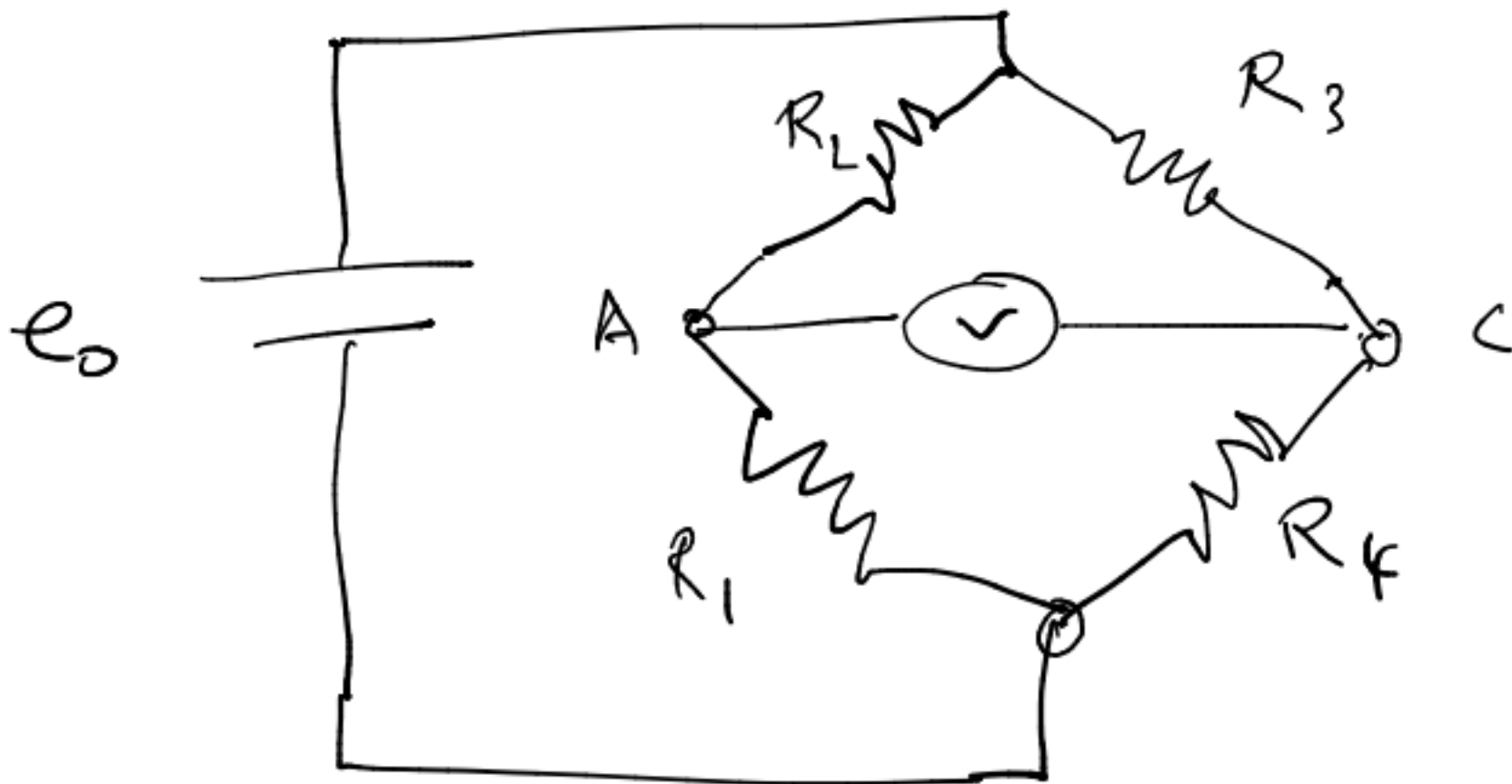

We start with a balanced bridge so  $\odot V$  leads zero at the beginning (prior to loading)

$$I - \frac{R_3}{R_3 + R_4} = I - \frac{R_2}{R_1 + R_2} \parallel \frac{R_4}{R_3 + R_4} = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow R_3 R_1 + \cancel{R_3 R_2} = \cancel{R_3 R_2} + R_2 R_4$$

$$\Rightarrow R_1 R_3 = R_2 R_4$$

Let the resistances change

$$R_1 \longrightarrow R_1 + \Delta R_1$$

$$R_2 \longrightarrow R_2 + \Delta R_2$$

$$R_3 \longrightarrow R_3 + \Delta R_3$$

$$R_4 \longrightarrow R_4 + \Delta R_4$$

$$e_0 \longrightarrow e_0 + \Delta e_0$$

Let the  $\odot$  reading be  $e$ .

In the balanced bridge  $e = 0$ .

We want a formula for

$\Delta e$  due to  $\Delta e_0, \Delta R_1, \dots, \Delta R_4$ .

$$e = V_C - V_A = \left( \frac{R_3}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) e_0$$

$$de = \frac{\partial e}{\partial R_1} dR_1 + \dots + \frac{\partial e}{\partial R_4} dR_4 + \frac{\partial e}{\partial e_0} de_0$$

$$\begin{aligned}
\frac{\partial e}{\partial R_1} &= -e_0 \frac{\partial}{\partial R_1} \left( \frac{R_2}{R_1 + R_2} \right) \\
&= -e_0 R_2 \frac{\partial}{\partial R_1} (R_1 + R_2)^{-1} \\
&= \frac{e_0 R_2}{(R_1 + R_2)^2} \frac{\partial}{\partial R_1} (R_1 + R_2) \\
&= \frac{e_0 R_2}{(R_1 + R_2)^2}
\end{aligned}$$

$$\frac{\partial e}{\partial R_1} dR_1 = \frac{e_0 R_2}{(R_1 + R_2)^2} dR_1$$

Similarly, get  $\frac{\partial e}{\partial R_2} dR_2$ , etc..

$$\Delta e = \frac{R_1 R_2 e_0}{(R_1 + R_2)^2} \left( \frac{\Delta R_1}{R_1} - \frac{\Delta R_2}{R_2} \right)$$

↑  
Volt  
meter  
reading

$$+ \frac{R_3 R_4 e_0}{(R_3 + R_4)^2} \left( \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4} \right)$$

$$+ \left( \frac{R_3}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) \Delta e_0$$

∴ bridge was initially balanced.

$$\Rightarrow \frac{\Delta e}{e_0} = \frac{R_1 R_2}{(R_1 + R_2)^2} \left( \frac{\Delta R_1}{R_1} - \frac{\Delta R_2}{R_2} \right) + \frac{R_3 R_4}{(R_3 + R_4)^2} \left( \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4} \right)$$

equal for a balanced bridge.

$$\Rightarrow \frac{\Delta e}{e_0} = \frac{R_1 R_2}{(R_1 + R_2)^2} \left\{ \frac{\Delta R_1}{R_1} - \frac{\Delta R_2}{R_2} + \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4} \right\}$$

$\left. \begin{array}{l} R_1 = R_2 \\ R_3 = R_4 \end{array} \right\}$  Note: Not demanding equality of  $\Delta R_1, \Delta R_2$  etc

$$\frac{\Delta e}{e_0} = \frac{1}{4} \left\{ \frac{\Delta R_1 - \Delta R_2}{R_1} + \frac{\Delta R_3 - \Delta R_4}{R_3} \right\}$$

↑ circuit factor

Quarter bridge

$R_1 \rightarrow$  strain gauge.

$R_1 \rightarrow R_1 + \Delta R_1$

$$\Delta R_2 = \Delta R_3 = \Delta R_4$$

$$\frac{\Delta e}{e_0} = \frac{1}{4} \frac{\Delta R_1}{R_1} = \frac{S \epsilon}{4}$$

$\frac{\Delta R}{R} = S \epsilon$





measured by  $\Delta e$  (circled),  $\frac{\Delta e}{e_0}$  (circled),  $\frac{S \epsilon}{4}$  (circled) → unknown → gauge factor.

applied e.m.f. →

$$\Rightarrow \epsilon = \frac{4}{S} \frac{\Delta e}{e_0}$$

for a quarter bridge.

Half bridge:

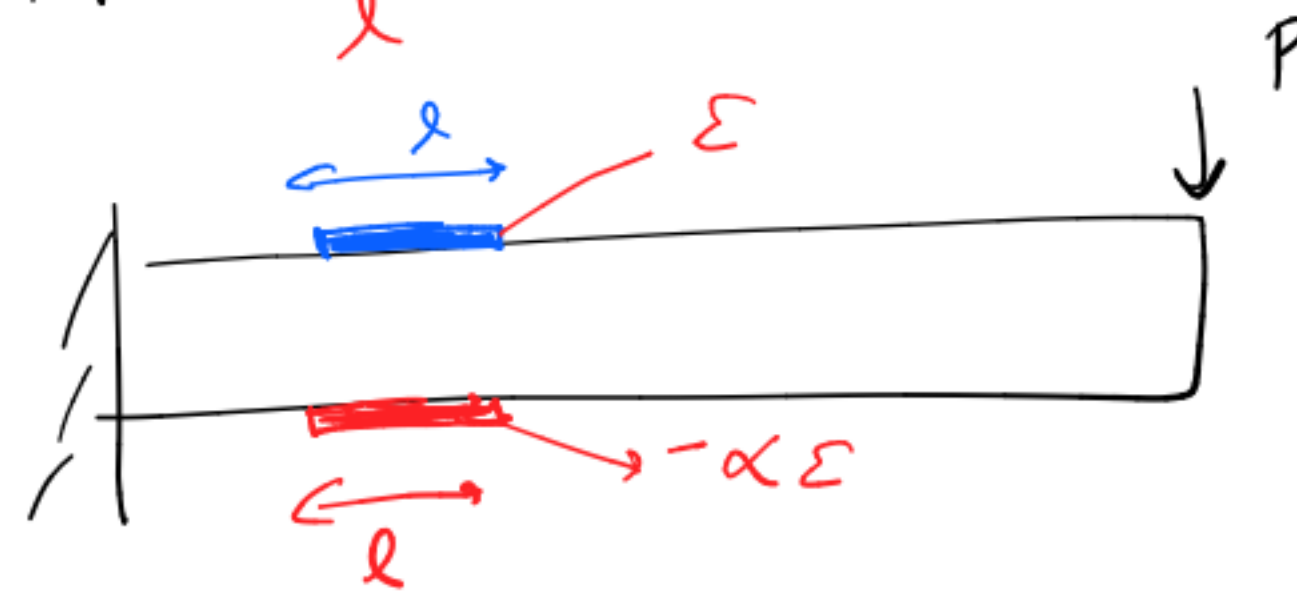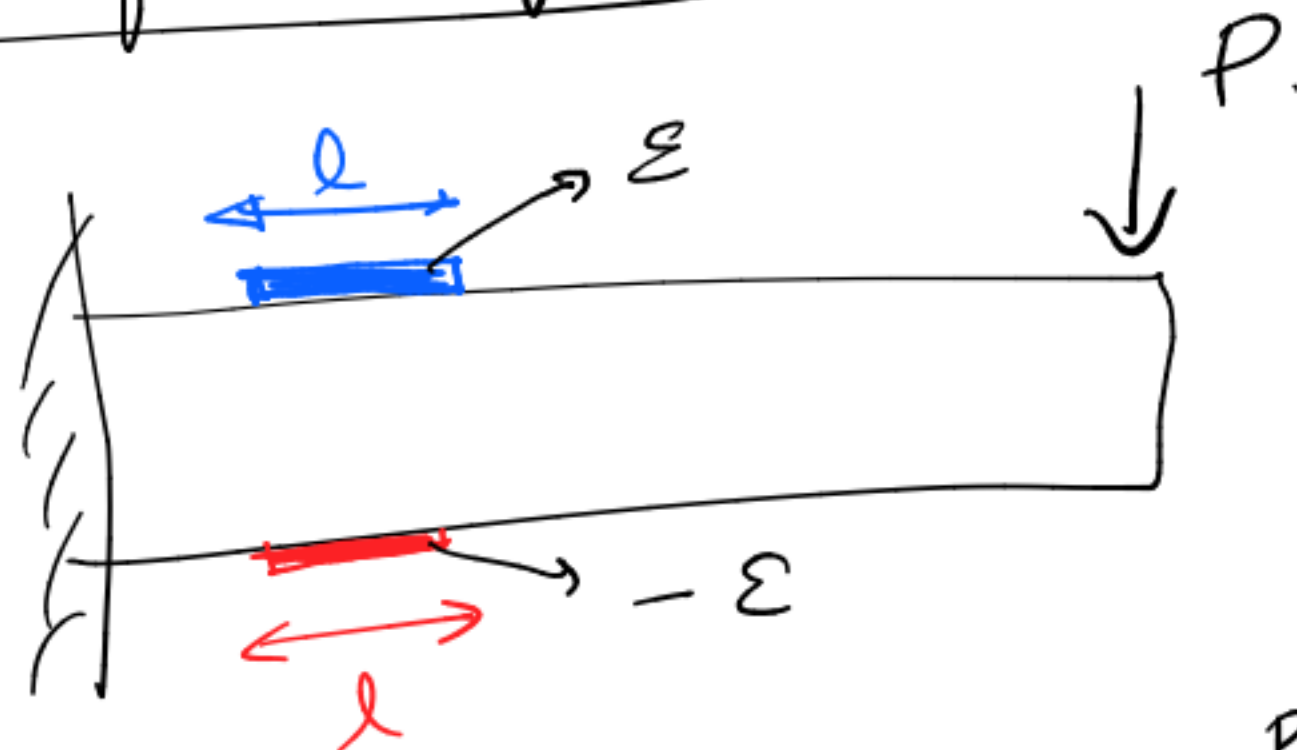

Let us assume the 2 SGs pick up  $\pm \epsilon$  strain.

Use this information in formula

(\*) of page 6.

$$\Delta R_1 = \Delta R_2 = 0.$$

$$\frac{\Delta R_3}{R_3} = S \epsilon$$

↑  
upper gauge

$$\frac{\Delta R_4}{R_4} = -S \epsilon$$

↑  
lower gauge

Coming from BSM theory.

$$\frac{\Delta e}{e_0} = \frac{1}{4} \{ 2 S \epsilon \} = \frac{1}{2} S \epsilon.$$

↑  
Sensitivity


↑  
applied emf

↑  
unknown strain


$$\epsilon = \frac{2}{S} \frac{\Delta e}{e_0}$$




Full bridge.

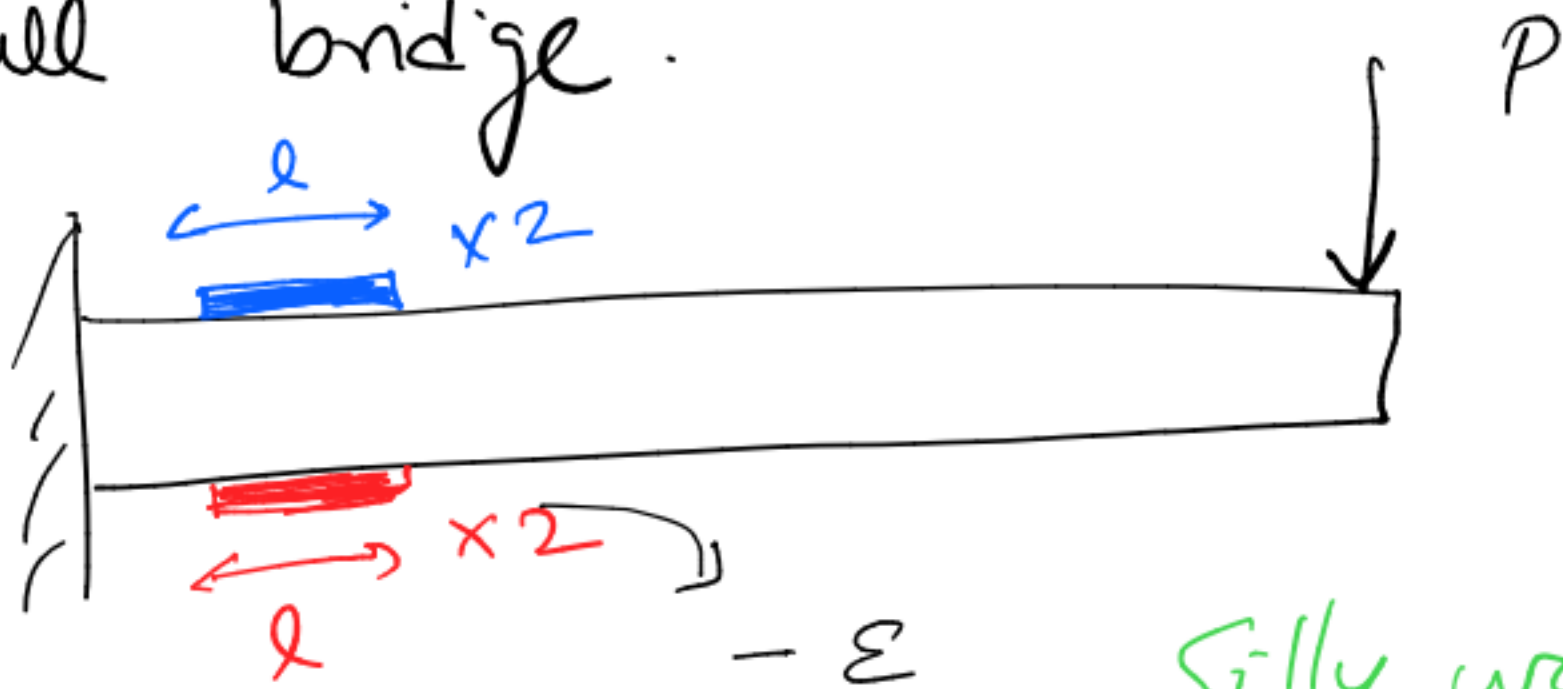

Top view:

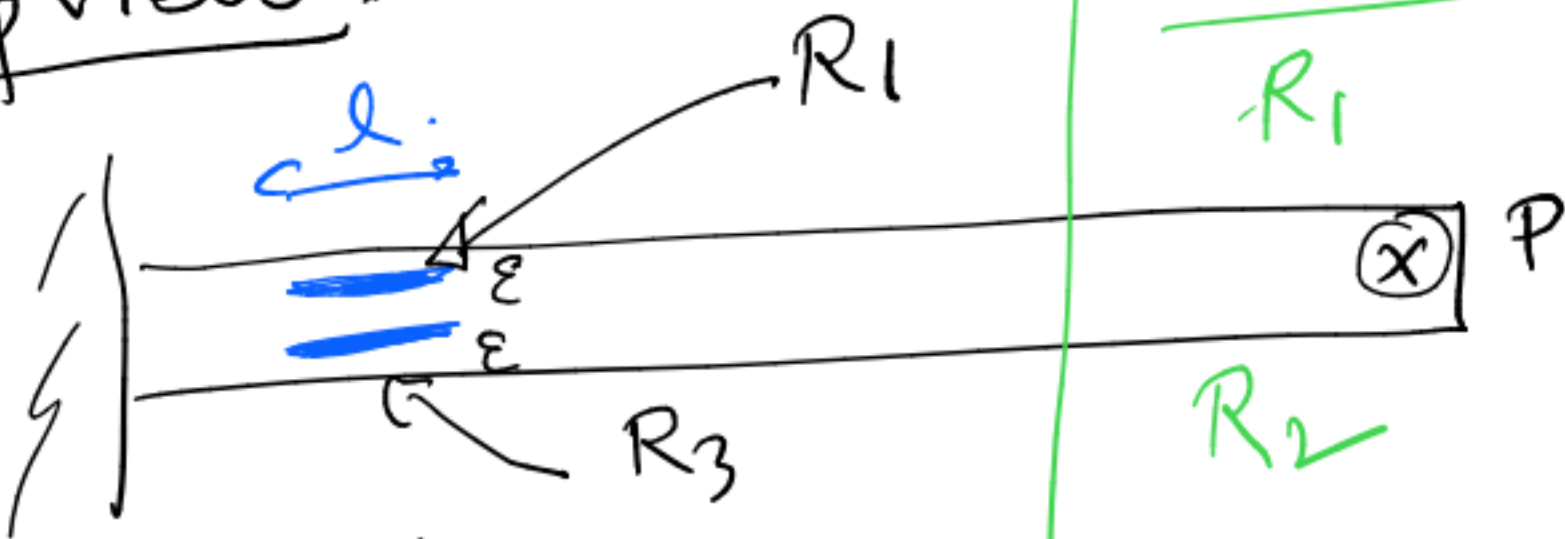

Bottom view:

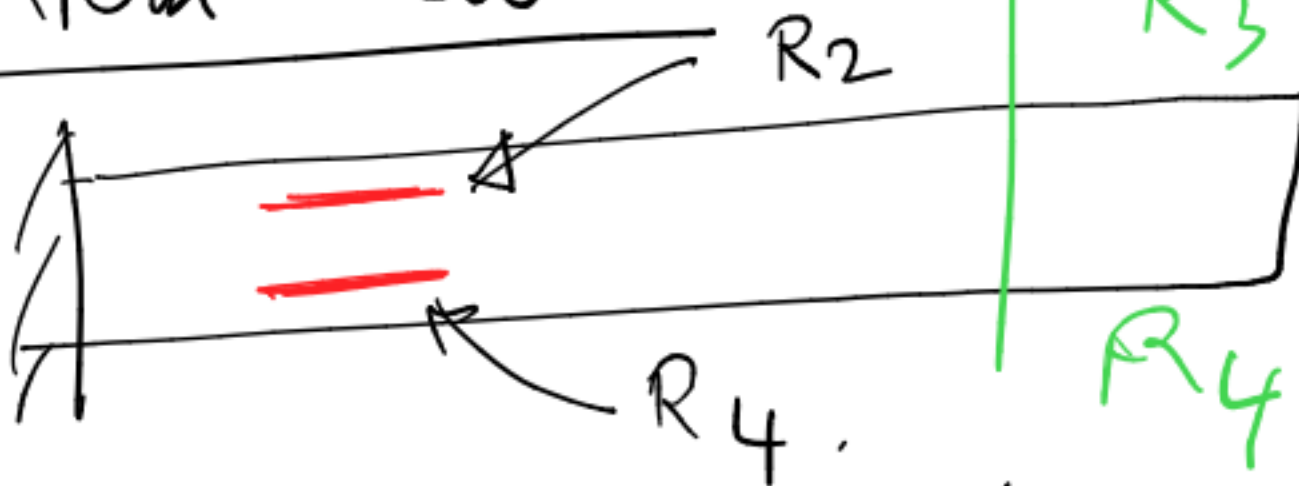

Silly way:

$R_1$

$R_2$

$R_3$


$R_4$

Using Eq (A) on page 6,

$$\frac{\Delta e}{e_0} = \frac{1}{4} \left\{ \cancel{4} S \epsilon \right\}$$


$$\Rightarrow \Sigma = \frac{1}{S} \frac{e}{e_0} \quad \text{for a full bridge.}$$

# Load Cell:

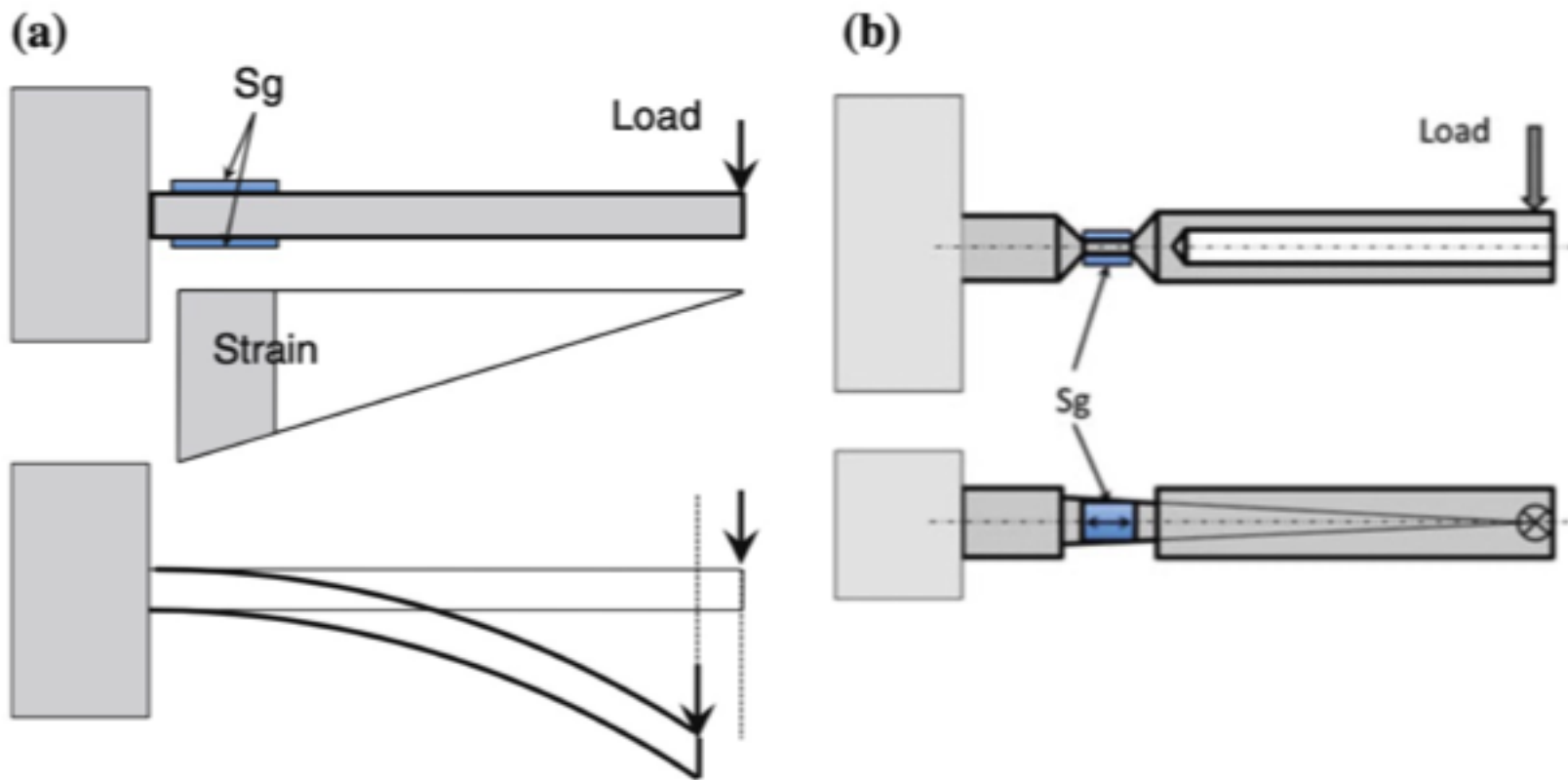

**Fig. 2.27** The simplest example of the bending cell. **a** A cantilever beam with a load at one end, instrumented with two opposing strain gages and **b** an improved development of the basic idea by reducing the thickness and tapering the measuring area in order to make the strains in the gage grid uniform

## Constrained beam:

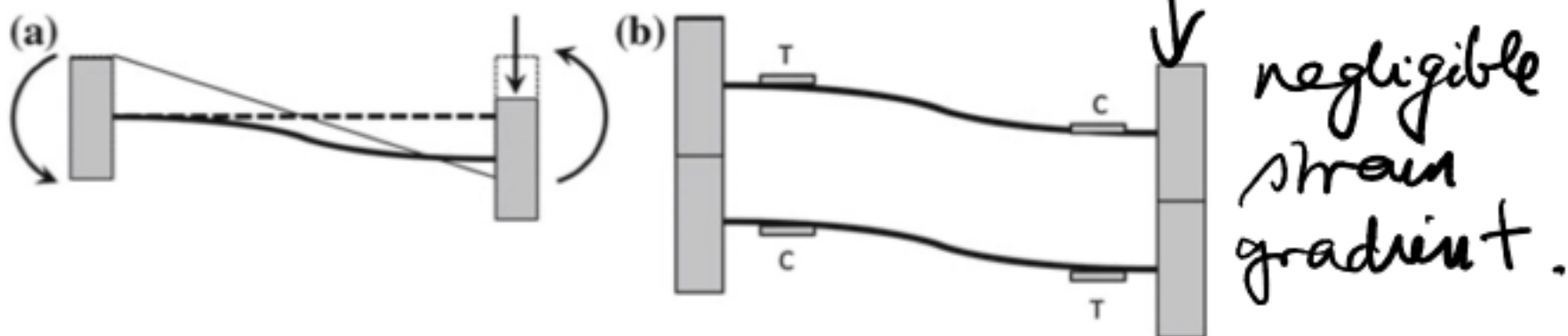

**Fig. 2.28** Static schemes of load cells with single beam: **a** doubly fixed, with loads and moments applied to the opposite ends and **b** with double beam, instrumented with four strain gages on the opposite sides

